
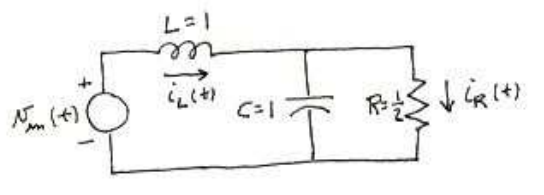


520.214 Signals and Systems, H13-08  
 Due Friday, May 2, 2008

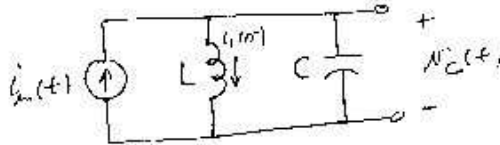
1. Consider the circuit shown below, where the input voltage is  $v_{in}(t) = u(t)$  and the initial conditions are  $i_L(0^-) = 1$ ,  $v_C(0^-) = 0$ . Compute the current through the resistor,  $i_R(t)$  for  $t \geq 0$ .



2. For the circuit shown below, with  $L = 1$  and  $C = 1$ , suppose the input current is  $i_{in}(t) = 2u(t)$ , the initial current in the inductor is  $i_L(0^-) = 1$  in the direction shown, and the initial voltage on the capacitor is zero. Compute the voltage output,  $v_C(t)$ .



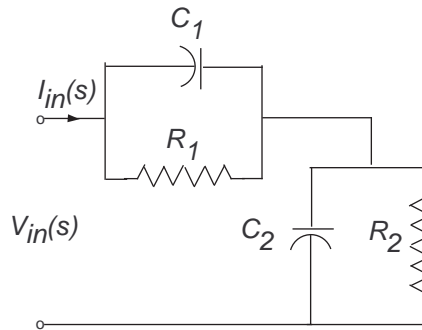3. Determine the input impedance  $Z_{in}(s)$  of this circuit:



- 5 For the system with transfer function

$$\frac{Y(s)}{X(s)} = \frac{s - 3}{(s + 4)^2}$$

compute the steady-state response  $y_{ss}(t)$ , the time function that  $y(t)$  approaches asymptotically, as  $t \rightarrow \infty$ , to the input signals

- (a)  $x(t) = e^{-3t}u(t)$
- (b)  $x(t) = e^{3t}u(t)$
- (c)  $x(t) = 2\sin(3t)u(t)$  (Skip calculation of the phase angle. Simply call it  $\theta$ .)
- (d)  $x(t) = \delta(t)$

(e)  $x(t) = u(t)$

*(Yes, I know that I promised this would include only circuits problems, but this last one is important, so I included it.)*