

State Holding and Sequential Circuit Design


Andreas G. Andreou
Pedro Julian

Electrical and Computer Engineering
Johns Hopkins University


<http://andreoulab.net>

*Lecture Notes adapted from Lecture 05 in
MIT 6.004 Computation Structures
<http://6004.csail.mit.edu/>*

and from Pedro Julian's VLSI class notes

 


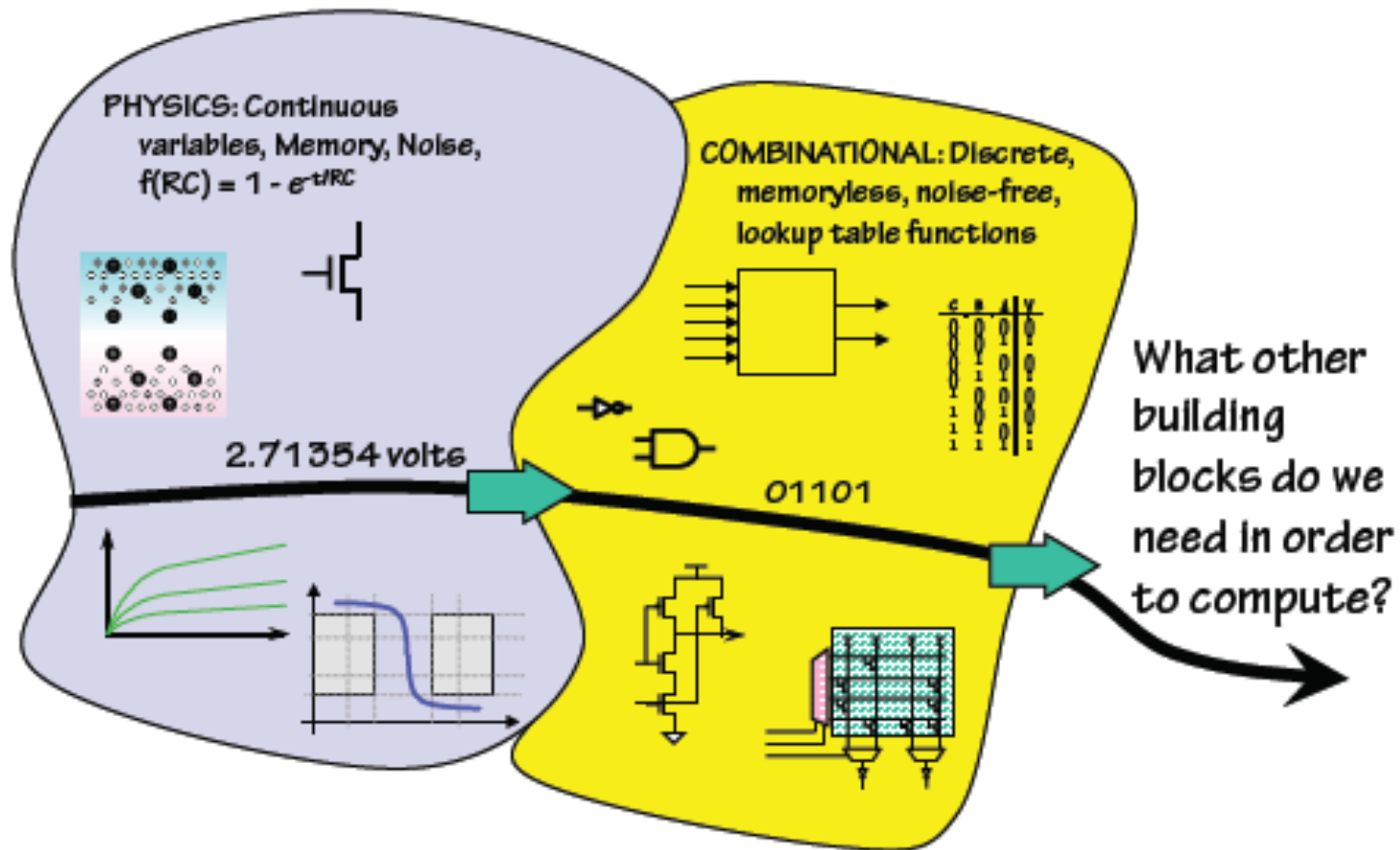Progress so far: all about levels of abstraction and representation



Something we can't build (yet)

 
What if you were given the following design specification:



What makes this circuit so different from those we've discussed before?

1. "State" – i.e. the circuit has memory
2. The output was changed by an input "event" (pushing a button) rather than an input "value"

Digital machine model

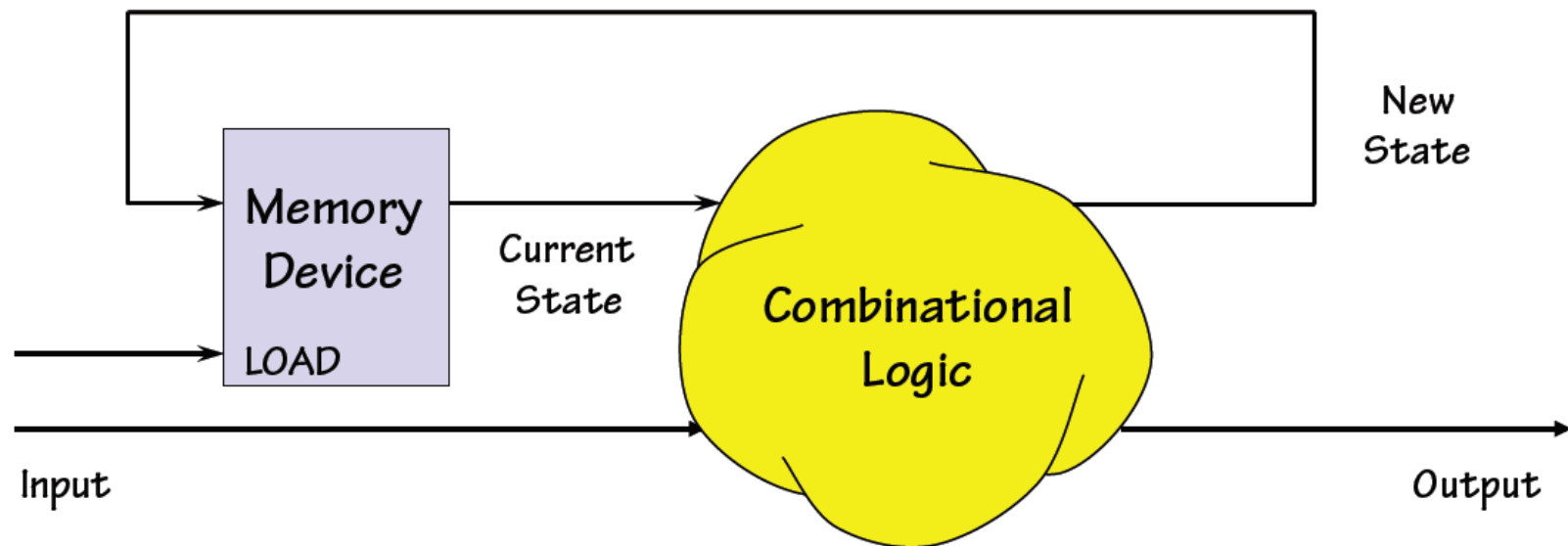

Plan: Build a Sequential Circuit with stored digital STATE –

- Memory stores CURRENT state, produced at output
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes on LOAD control input

Storage



Combinational logic is *stateless*:

valid outputs always reflect current inputs.

To build devices with state, we need components which *store* information (e.g., state) for subsequent access.

ROMs (and other combinational logic) store information “wired in” to their truth table


Read/Write memory elements are required to build devices capable of changing their contents.

How can we store – and subsequently access -- a bit?

- Mechanics: holes in cards/tapes
- Optics: Film, CDs, DVDs, ...
- Magnetic materials
- Delay lines; moonbounce
- Stored charge

Dynamic Storage: using capacitors

“store” a charge on a capacitor!

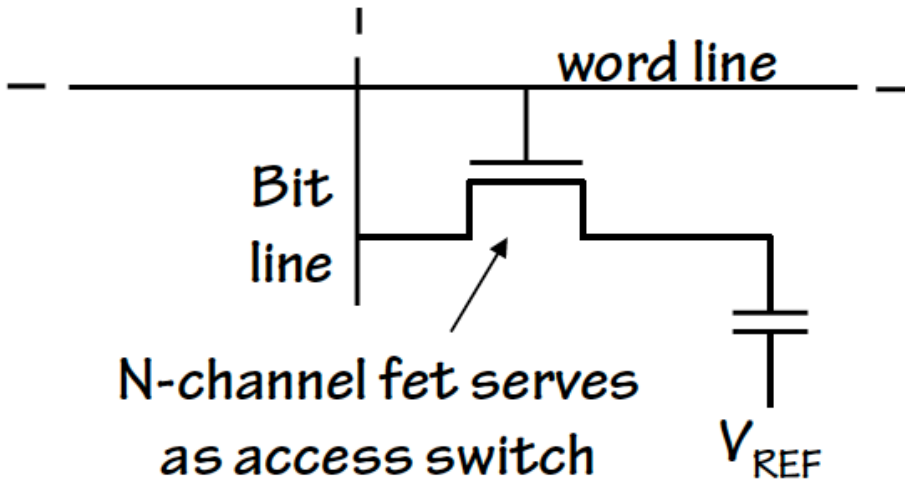

To write:



Drive bit line, turn on access fet,
force storage cap to new voltage

To read:


precharge bit line, turn on access f
detect (small) change in bit line vol

e-DRAM cell

Need cell with big capacitance !

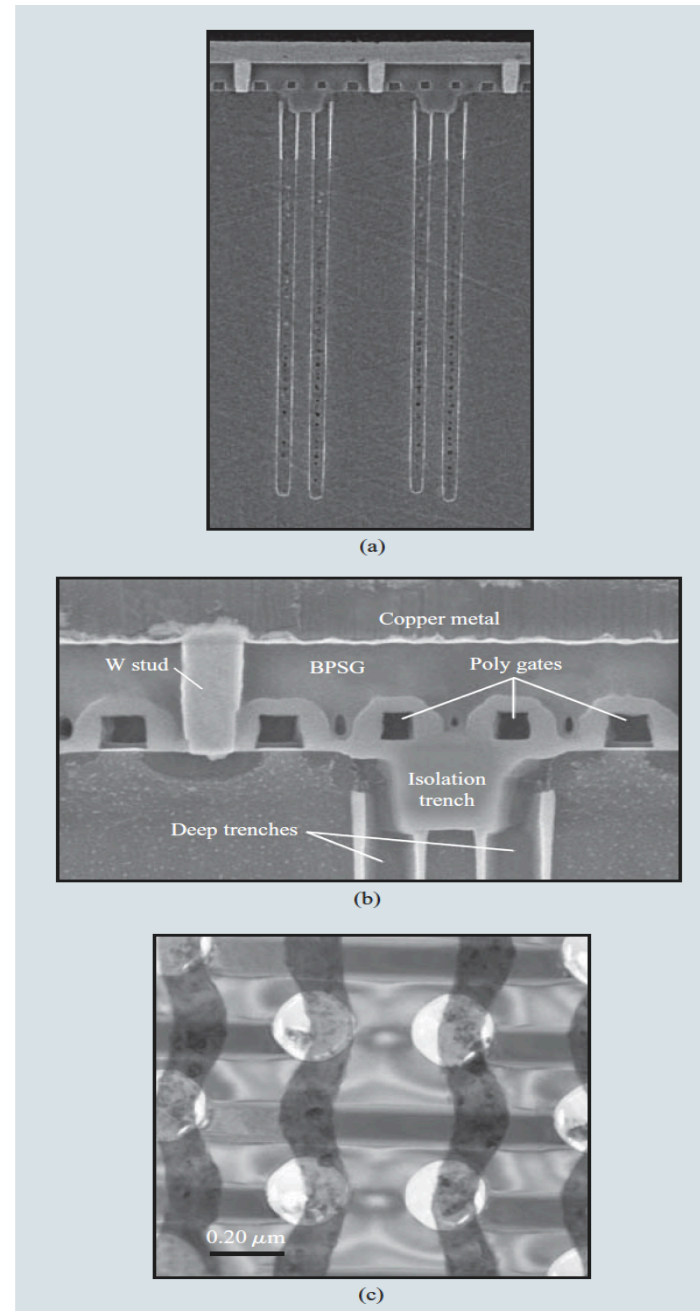 

Dynamic Storage: using capacitors

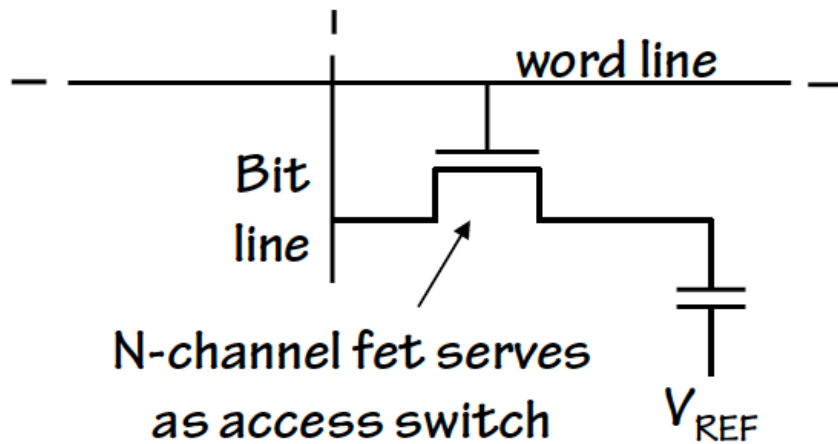


Pros:

- ◆ compact – low cost/bit (on BIG memories)


Cons:

 - ◆ complex interface
- ◆ stable? (noise, ...)
- ◆ it leaks! \Rightarrow refresh




Static Storage: using feedback

 IDEA: use **positive feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!



Result: a **bistable storage element**

 

Three solutions:


- ◆ two end-points are **stable**
- ◆ middle point is unstable

Not affected
by noise

We'll get back to this!

Settable storage element


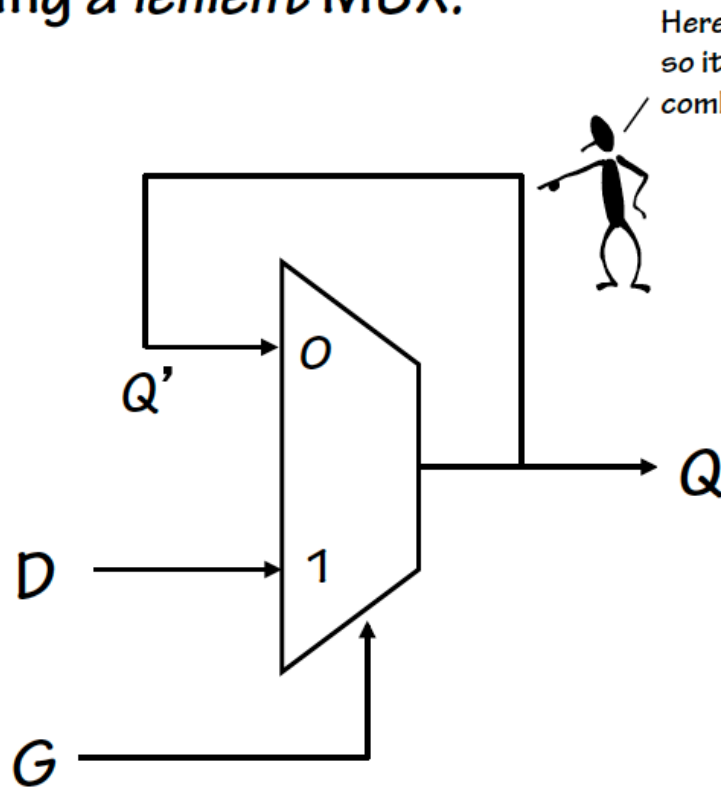
It's *easy* to build a *settable storage element* (called a **latch**) using a *lenient* MUX:



If $G=1$ Q follows D



If $G=0$ $Q' = Q$ (stable)

New device: "transparent" D latch

  



$G=1$:
Q follows D

$G=0$:
Q holds

 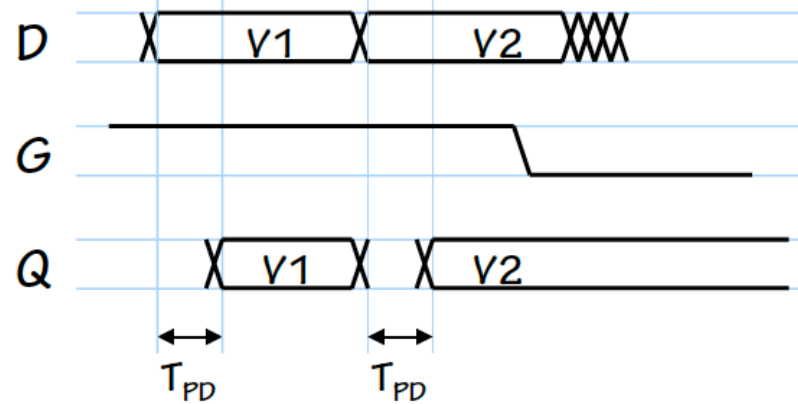



Latch: CMOS realization

  - Switches implemented using transmission gates
- Switches are complementary
 - L1 passes input to output in transparent mode
 - L2 closes loop and keeps the state





CMOS latches: types


► Positive

  

Negative

  

Let's try it out!

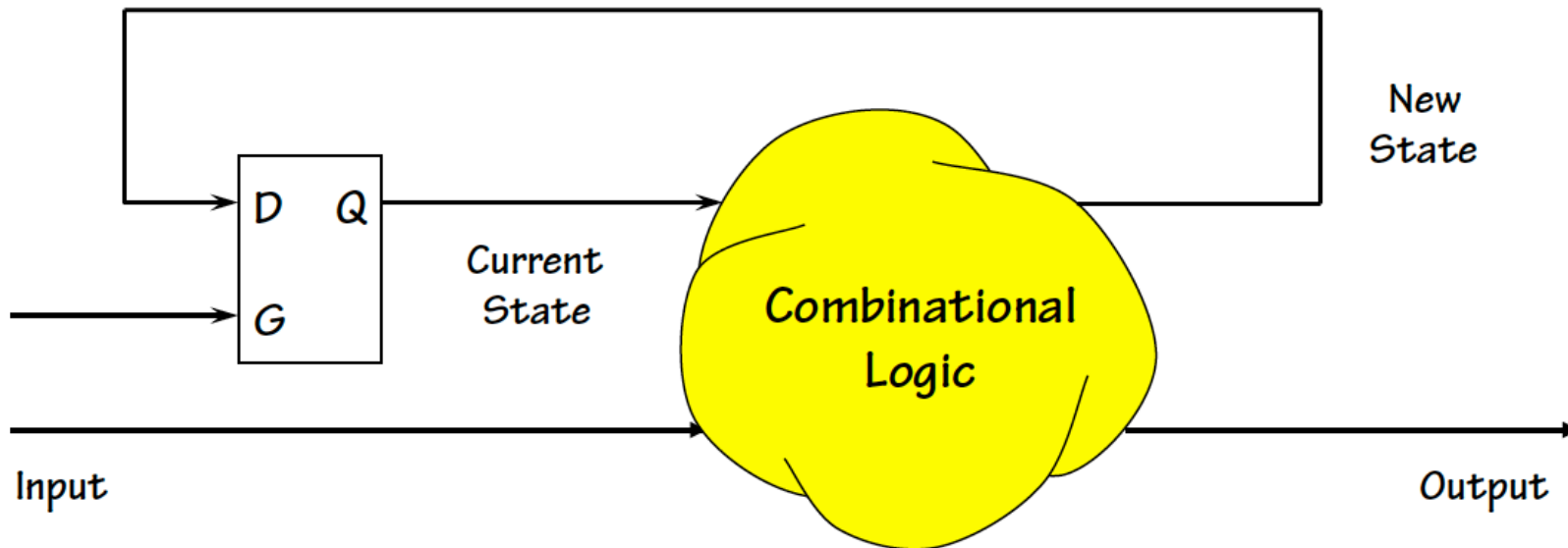


Plan: Build a Sequential Circuit with one bit of STATE -

- Single latch holds CURRENT state
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes when $G = 1$ (briefly!)

What happens when $G=1$?



Combinational cycles

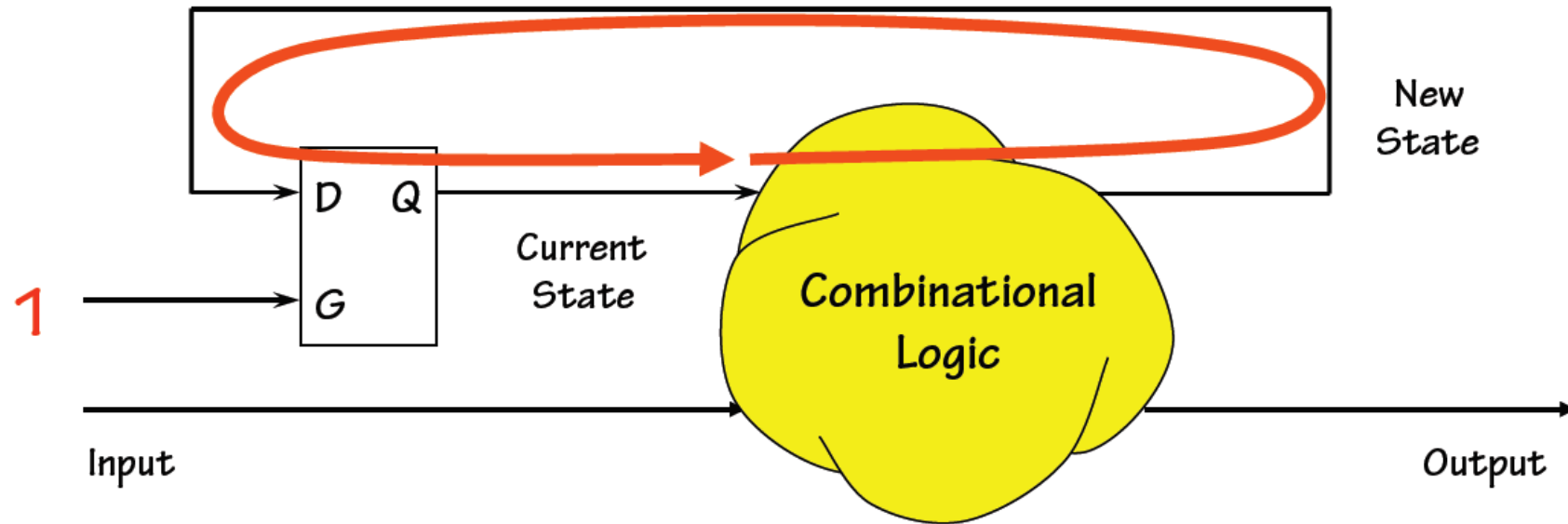

When $G=1$, latch is *Transparent*...

... provides a combinational path from D to Q.

Can't work without tricky timing constraints on $G=1$ pulse:

- Must fit within contamination delay of logic
- Must accommodate latch setup, hold times

Want to signal an INSTANT, not an INTERVAL...

Looks like a stupid
Approach to me...



Edge-triggered Flip-Flop

Transitions mark
instants, not intervals





$G = 0$

$0 \rightarrow 1$

$G = 1$



Master latch

Slave latch

  


Master latch

Slave latch

  

Edge-triggered Flip-Flop

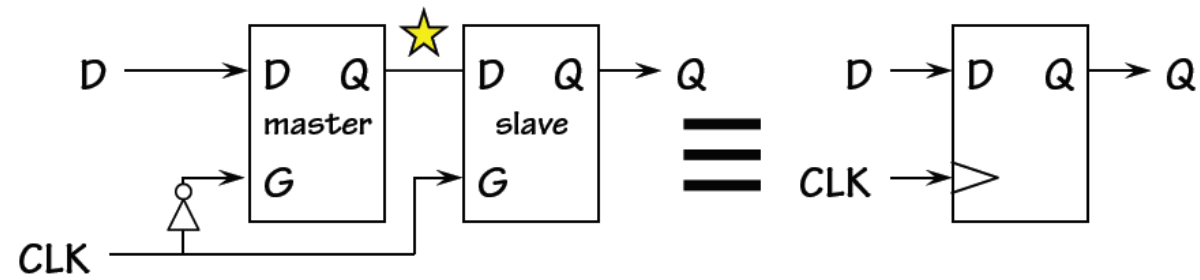

Observations:


- ♦ only one latch “transparent” at any time:
 - ♦ master closed when slave is open
 - ♦ slave closed when master is open
- ⇒ no combinational path through flip flop

(the feedback path in one of the master or slave latches is always active)

- ♦ Q only changes shortly after 0 → 1 transition of CLK, so flip flop **appears** to be “triggered” by rising edge of CLK





Flip-Flop waveforms

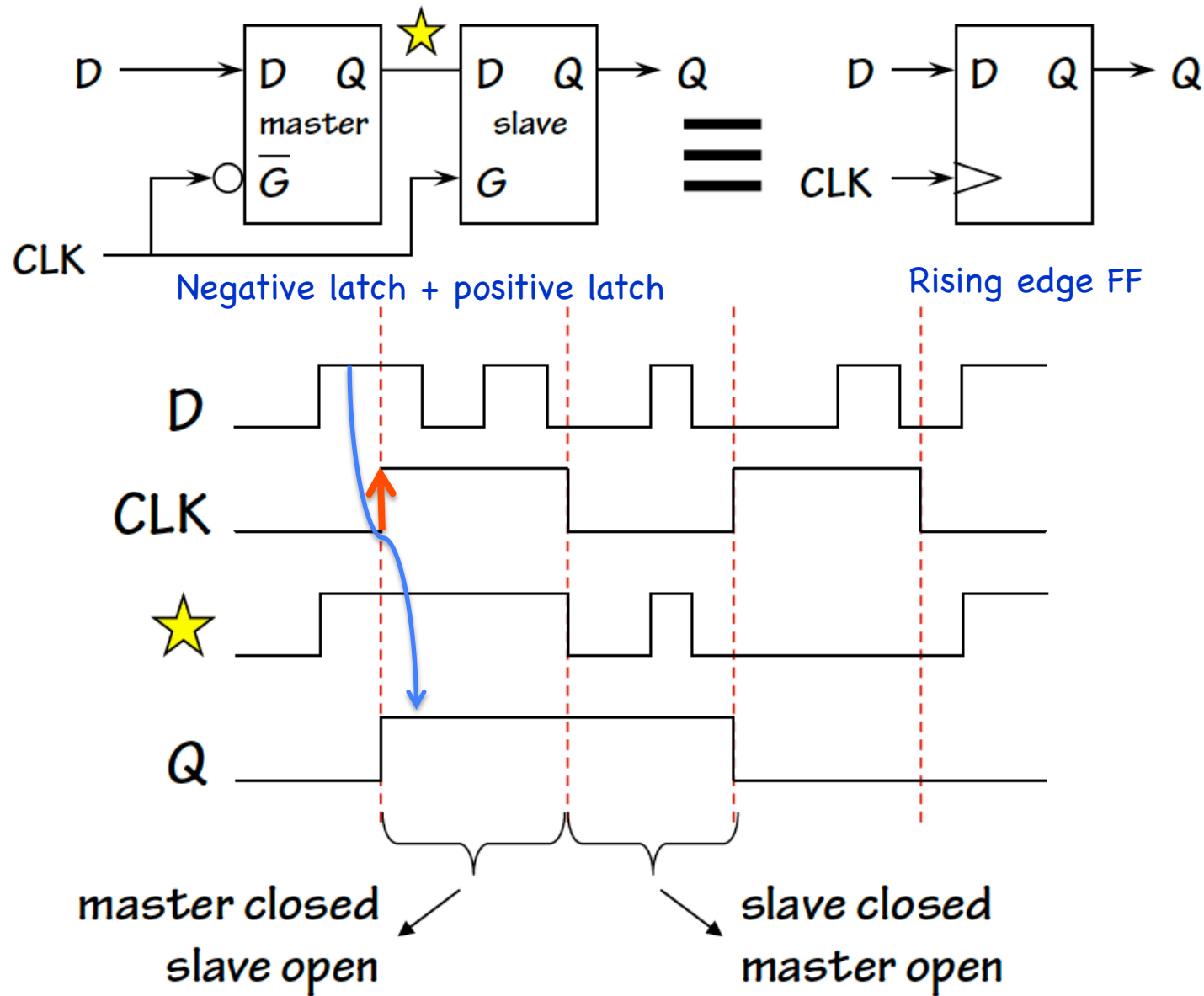



Edge triggered FF

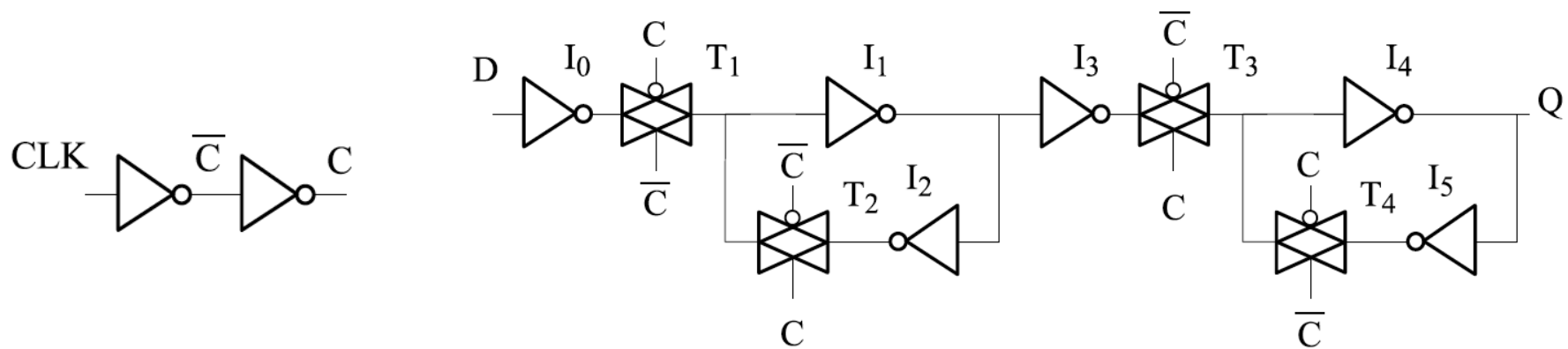 - Positive (rising) edge FF
 - Master negative, slave positive




Edge triggered FF

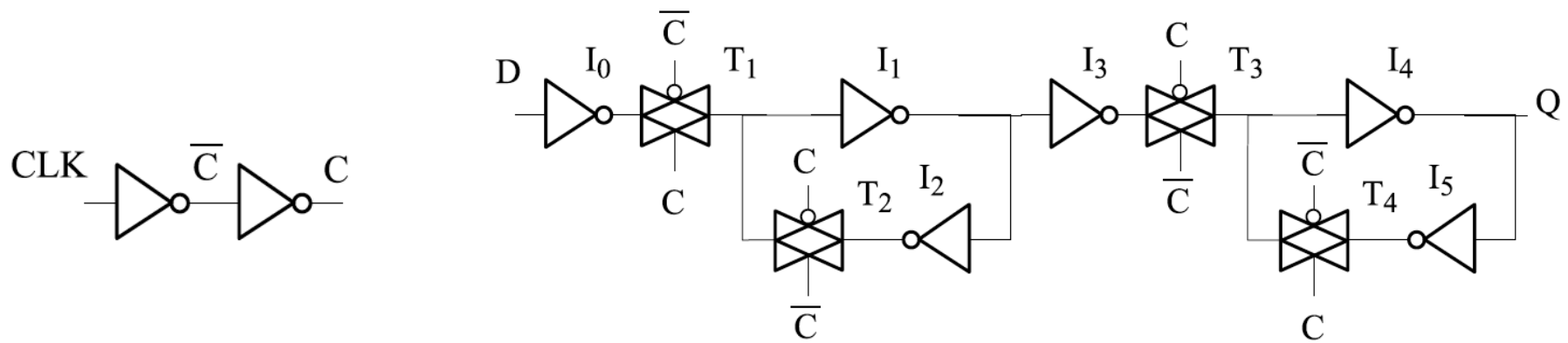 - Falling (negative) edge FF
 - Master positive, slave negative



Single-clock synchronous circuits

 


We'll use Flip Flops and *Registers* – groups of FFs sharing a clock input – in a highly constrained way to build digital systems:

Single-clock Synchronous Discipline

- No combinational cycles
- Single periodic clock signal shared among all clocked devices
- Only care about value of register data inputs just before rising edge of clock
- Period greater than every combinational delay + setup time
- Change saved state after noise-inducing logic transitions have stopped!

Model: Discrete Time

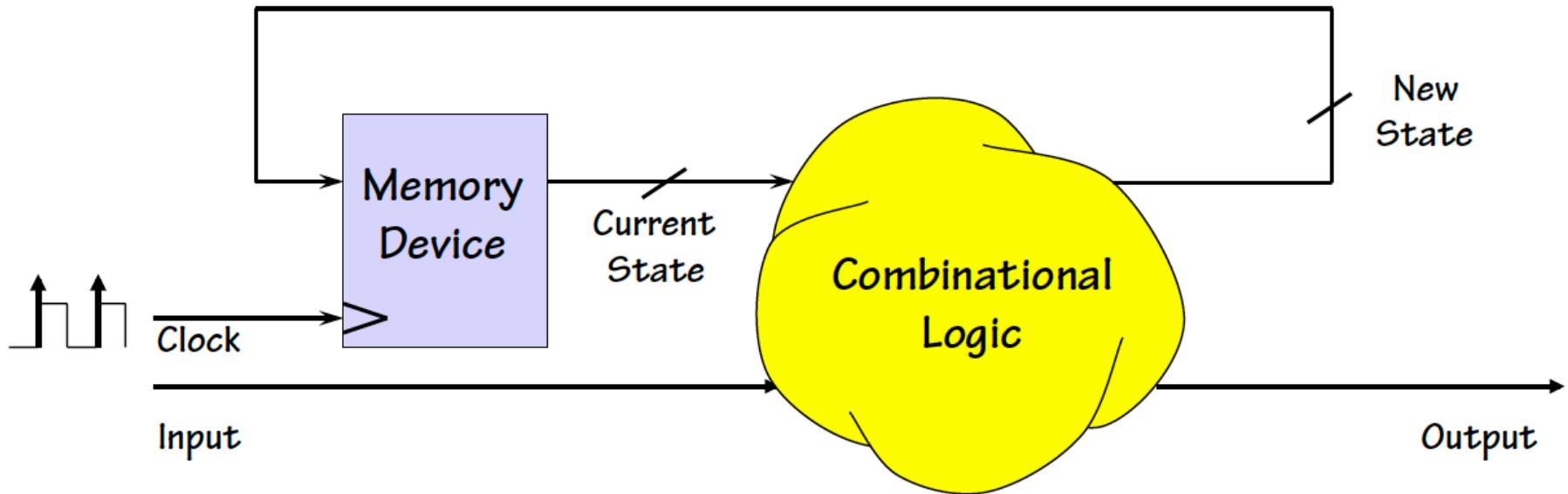

Active Clock Edges punctuate time ---

- Discrete Clock periods
- Discrete State Variables
- Discrete specifications (simple rules – eg tables – relating outputs to inputs, state variables)
- **ABSTRACTION: Finite State Machines (next lecture!)**

Summary

“Sequential” Circuits (with memory):

Basic memory elements:




- Feedback, detailed analysis => basic level-sensitive devices (eg, latch)
- 2 Latches => Flop
- Dynamic Discipline: constraints on input timing

Synchronous 1-clock logic:

- Simple rules for sequential circuits
- Yields clocked circuit with T_S, T_H constraints on input timing

Finite State Machines

Next Lecture Topic!

  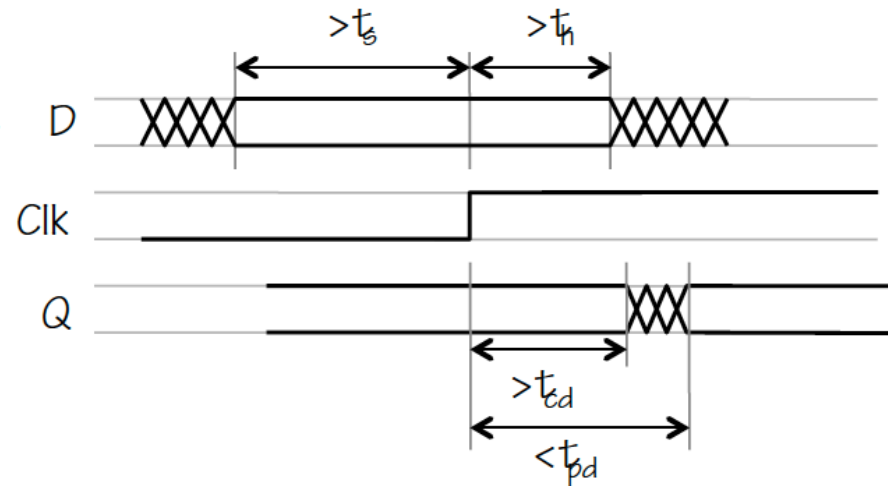

Computer Aided Design Tools

